

Task-2

Figure:1. Schematic Diagram of Traffic light of Aurdino in KiCad

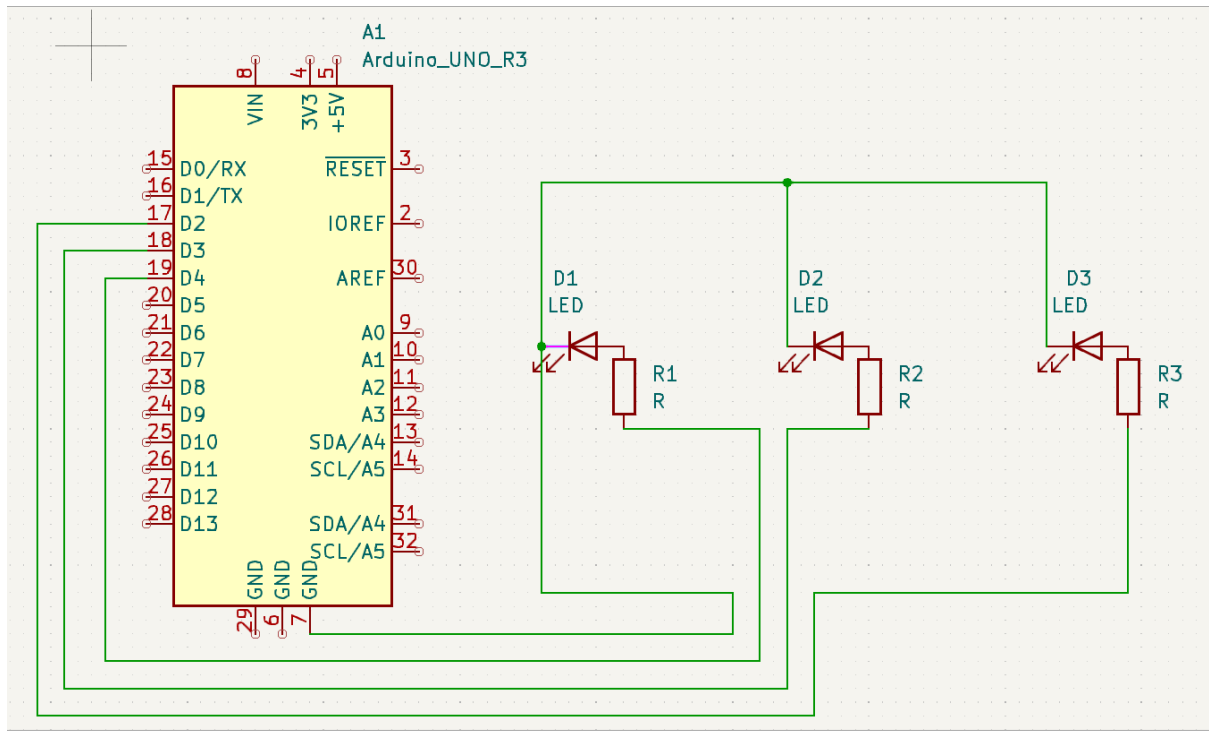


Figure:2.PCB with no DRC error

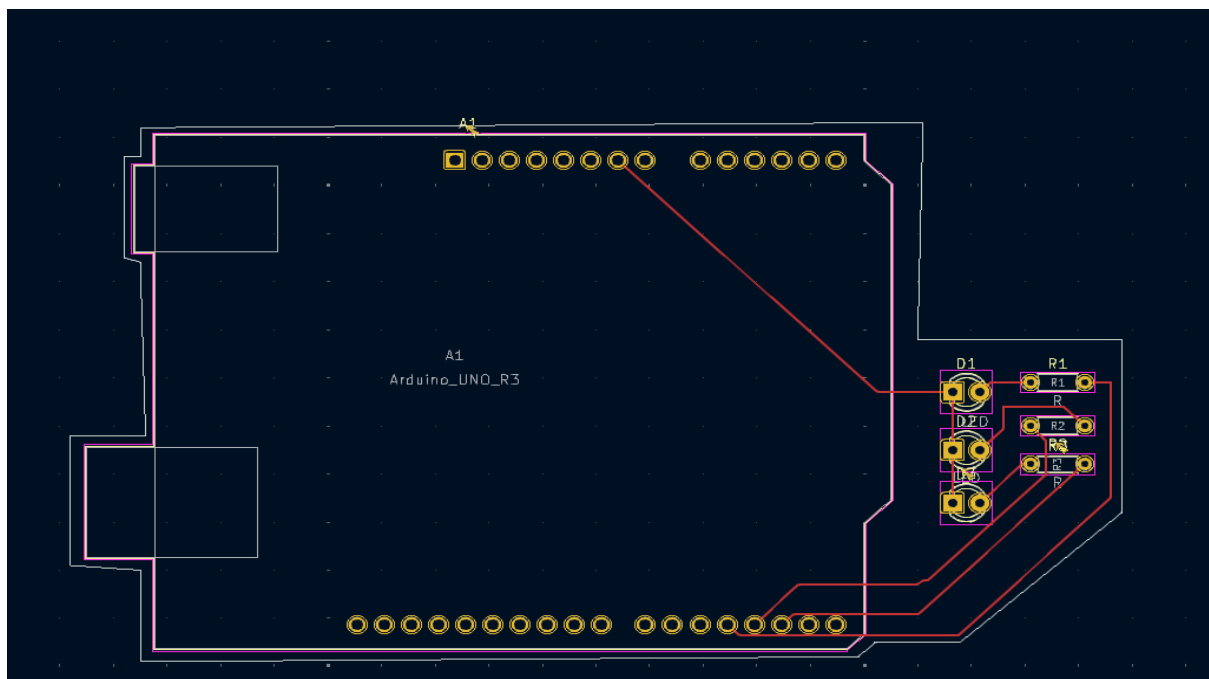


Figure: 3.DRC Check

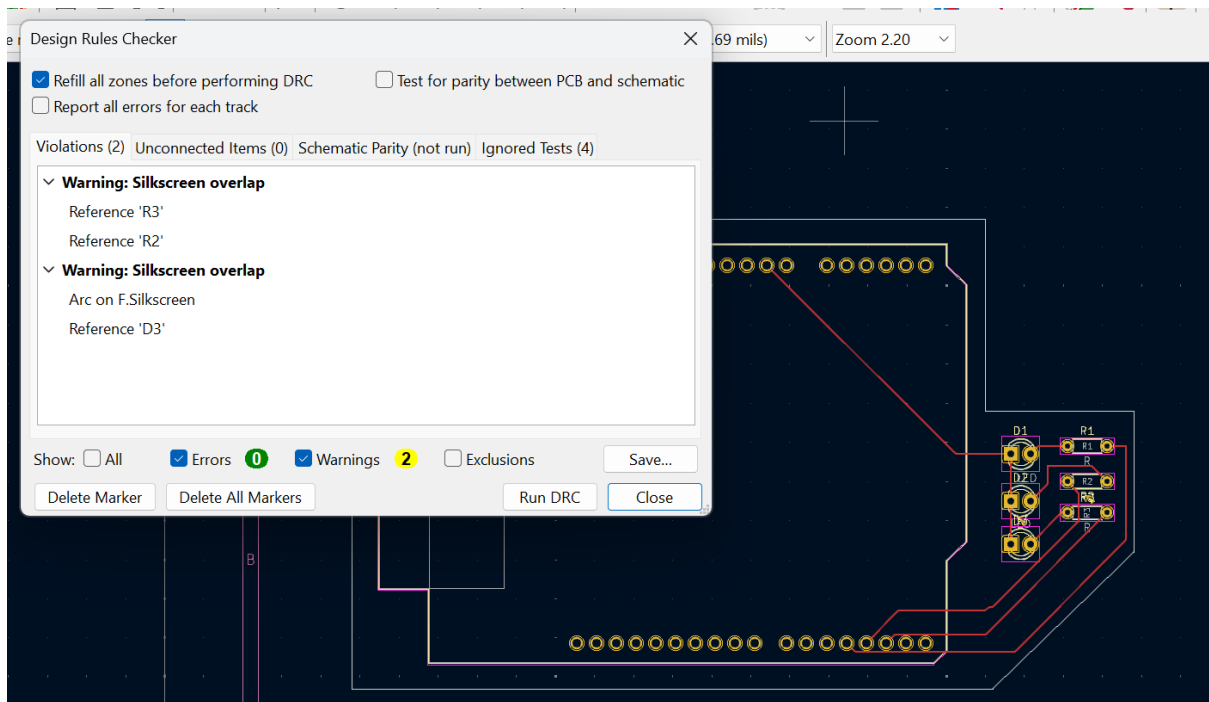


Figure: 4.3D View of Traffic light PCB

